

Wireline Data Transmission and Reception

Xavier Ramus

High-Speed Products

ABSTRACT

Many types of wires are widely used to transmit data. Specifically, Category 3 and Category 5 (Cat3 and Cat5e, respectively)—also known as *unshielded twisted pair* or UTP lines—are now recommended for new telephone installations. Coaxial (coax) cables are used to distribute cable television (CATV) signals throughout a home. #12 and #14 American wire gauge (AWG) electric power distribution wire is also used for powerline communication applications such as Homeplug™. Because of the wide availability and comparatively low cost, these media can also be used for point-to-point communications and data transmission for remote applications. Each of these media types shares a common characteristic: for a given cable length, the high-frequency components of a given signal will be attenuated more than the low-frequency components. This application note describes a possible system architecture for transmitting a signal with high-frequency content, compensating for the frequency-dependent attenuation, and receiving this type of signal for further processing.

Contents

1	Introduction	2
2	High-Level Signal Chain	2
3	Implementation Example	7
4	Conclusion	9

List of Figures

1	Attenuation vs Frequency for Cat5e and 75Ω Coax Cables	2
2	High-Level Signal Chain Block Diagram	2
3	Output Voltage and Current Limitations (OPA2673)	3
4	Typical Application Driver Circuits	4
5	Differential Equalizer Circuit	5
6	Single-Ended Equalizer Circuit.....	6
7	Differential Equalizer Circuit (VCA820)	6
8	Equalizer Circuit for 100ft of Belden 1694F Coax Cable	6
9	Cable Equalization and Cable Attenuation Comparison	7
10	Twisted Pair Evaluation Circuit Model.....	7
11	Belden 8723 Shielded Twisted-Pair Frequency Response.....	7
12	Proposed Tx and Rx Schematic	8
13	Theoretical Gain Matching to the Attenuation	8
14	Developed Tx and Rx Circuit with the OPA683.....	9
15	Measured Circuit Performance	9

List of Tables

1	Dual Amplifiers for Use as Twisted-Pair Drivers	3
2	Single Amplifiers for Use as Coax Cable Drivers	3
3	Dual Amplifiers for Differential I/O Receiver Functions	4
4	Fully-Differential Amplifiers for Differential I/O Receiver Functions	5

Homeplug is a trademark of HomePlug Powerline Alliance, Inc.
All other trademarks are the property of their respective owners.

5	Single-Ended Amplifiers for I/O Receiver Functions	5
---	--	---

1 Introduction

Two of the most widely-used wireline families are the coax cable and the Cat5e UTP cable. Typical attenuation characteristics for one cable from each family is represented in [Figure 1](#). Both of these common cables are available from a variety of manufacturers. The cables measured in [Figure 1](#) are manufactured by Belden and have been normalized to a length of 100m. Note that the 75Ω coax cable attenuation shown here is a nominal attenuation, whereas the Cat5e attenuation is a maximum attenuation.

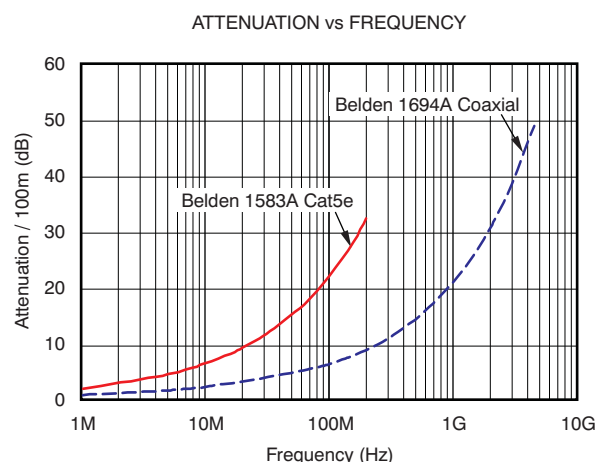


Figure 1. Attenuation vs Frequency for Cat5e and 75Ω Coax Cables

Now that we have a description of how the medium affects the signal integrity, we can start looking at a general block diagram of the signal chain.

2 High-Level Signal Chain

At the simplest level, for a system that requires only data transmission from board A to board B, [Figure 2](#) presents a straightforward description.



Figure 2. High-Level Signal Chain Block Diagram

2.1 Transmitter

The transmitter consists of a transmission amplifier, whose function is to amplify the signal and drive the line. In addition to frequency response and quiescent current, the two most important parameters to consider when selecting a transmission amplifier are output voltage swing and output current capability. These two parameters are interdependent; therefore, a V-I curve (or output voltage versus output current capability) should be among the first parameters looked at when selecting this amplifier component. The V-I curve for the [OPA2673](#) is shown in [Figure 3](#) as an example.

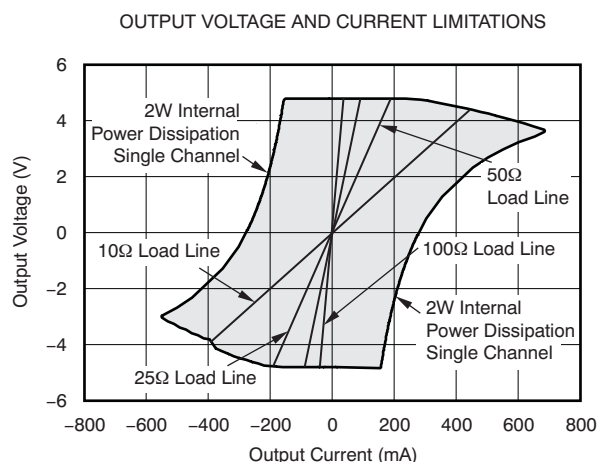


Figure 3. Output Voltage and Current Limitations (OPA2673)

In general, for high-speed wireline applications, a current feedback amplifier (CFA) is more appropriate than a voltage feedback amplifier (VFA) as a result of the high slew rate advantage generally offered by the CFA. Additionally, dual amplifiers are used more often for twisted-pair installations, where a differential signal is required; single amplifiers, on the other hand, are generally used more often with coax cable, where single-ended termination is more common.

For differential twisted-pair signal driving, the amplifiers listed in [Table 1](#) are recommended. These amplifiers are a selection of the many devices currently available from TI. Refer to the DSL/Powerline Amplifier selection page on the TI web site at www.ti.com for a more complete list.

Table 1. Dual Amplifiers for Use as Twisted-Pair Drivers

Amplifier	Output Voltage into 100Ω Load (V)	Output Current (mA)	Quiescent Current (mA)	Bandwidth at $G = +2V/V$ (MHz)
OPA2695	± 3.9 ($V_S = \pm 5V$)	± 120	25.8	850
OPA2673	± 4.8 ($V_S = \pm 6V$)	± 700	32	450
OPA2674	± 5.0 ($V_S = \pm 6V$)	± 500	18	225
OPA2691	± 3.9 ($V_S = \pm 5V$)	± 190	10.2	225
OPA2683	—	$+150/-110$	1.88	150
THS6043	± 10.8 ($V_S = \pm 12V$)	± 350	16.4	95
THS6182	± 13.9 ($V_S = \pm 15V$)	± 600	23	80

For single-ended applications, such as a coax cable driver, the amplifiers listed in [Table 2](#) can be used.

Table 2. Single Amplifiers for Use as Coax Cable Drivers

Amplifier	Output Voltage into 100Ω Load (V)	Output Current (mA)	Quiescent Current (mA)	Bandwidth at $G = +2V/V$ (MHz)
OPA695	± 3.9 ($V_S = \pm 5V$)	± 120	12.3	850
OPA691	± 3.9 ($V_S = \pm 5V$)	± 190	5.1	225
THS3001	± 12.8 ($V_S = \pm 15V$)	± 120	6.6	385
THS3091	± 12.5 ($V_S = \pm 15V$)	$+280/-250$	9.5	210

Typical application circuits for both types of drivers are shown in [Figure 4a](#) (for twisted pair) and [Figure 4b](#) (for coax).

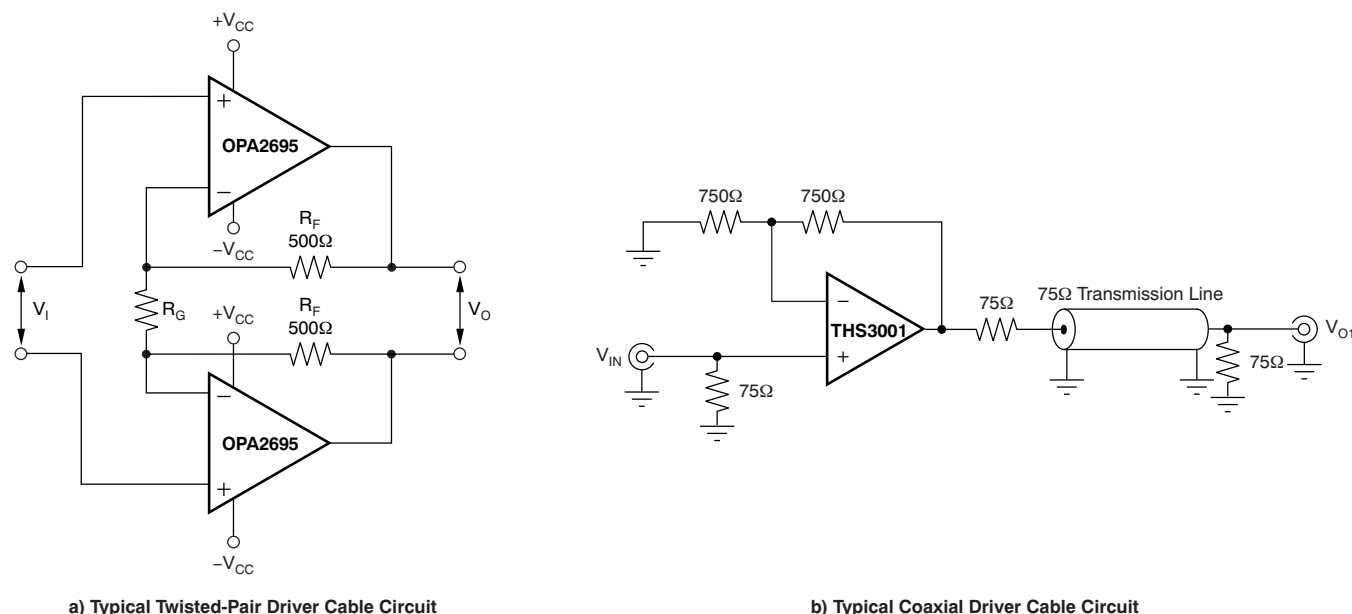


Figure 4. Typical Application Driver Circuits

Note that although it is possible to compensate the line attenuation by peaking the frequency response of the line driver, this technique is not normally implemented in practice for a couple of reasons. First, this compensation implies that a fixed cable length is used. Second, if the media are unshielded, the high-frequency content of the signal will be amplified and generate more radiation, which could contradict or violate applicable emissions standards.

2.2 Receiver

On the receiver side, depending on the maximum frequency component, the nature of the signal, and the length of the transmission line, there are two primary implementation approaches.

1. Take the loss inherent to the transmission line; or
2. Compensate the signal loss. This approach is normally referred to as *equalization*.

VFAs are normally used for this role because they traditionally provide lower input voltage noise and better dc precision. If the signal processing is single-ended or differential, there are several available options.

First, for differential processing, both dual amplifiers and fully-differential amplifiers can be used. A dual amplifier in the same configuration as the line driver (see [Figure 4a](#)) can more easily provide better back-matching over frequency because the amplifier input is high impedance. [Table 3](#) provides a short selection guide for this type of device.

Table 3. Dual Amplifiers for Differential I/O Receiver Functions

Amplifier	Input Voltage Noise (nV/√Hz)	Bandwidth at Gain (MHz)
OPA2695	1.8	850 (2V/V)
OPA2690	5.5	220 (2V/V)
OPA2822	2	200 (2V/V)
OPA2846	1.2	300 (10V/V)
THS4012	7.5	290 (1V/V)
THS4022	1.5	350 (10V/V)

Note that if very wideband performance is required, CFAs may be a better option here.

Fully-differential amplifiers are also a very good option for fully-differential I/O. [Table 4](#) lists a selection of amplifiers that meet this requirement.

Table 4. Fully-Differential Amplifiers for Differential I/O Receiver Functions

Amplifier	Input Voltage Noise ($\text{nV}/\sqrt{\text{Hz}}$)	Bandwidth at Gain (MHz)
THS4509	1.9	2000 (2V/V)
THS4513	2.2	1400 (2V/V)
THS4503	6.8	175 (2V/V)
THS4520	2	450 (2V/V)
THS4521	4.6	135 (1V/V)

For single-ended application, [Table 5](#) provides a quick selection guide.

Table 5. Single-Ended Amplifiers for I/O Receiver Functions

Amplifier	Input Voltage Noise ($\text{nV}/\sqrt{\text{Hz}}$)	Bandwidth at Gain (MHz)
OPA695	1.8	850 (2V/V)
OPA690	5.5	220 (2V/V)
OPA820	2.2	200 (2V/V)
OPA846	1.2	300 (10V/V)
THS4011	7.5	290 (1V/V)
THS4021	1.5	350 (10V/V)

Receiving the signal with an amplifier is the simplest configuration, and works well for short distances and fairly low frequencies without any issues. At high frequencies, however, an unprocessed signal can benefit from equalization. An equalizer circuit is a circuit that compensates for any transmission losses. This technique can be achieved with operational amplifiers, as [Figure 5](#) illustrates.

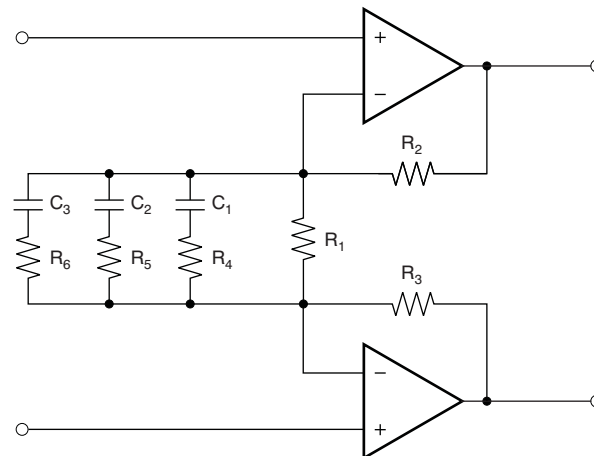


Figure 5. Differential Equalizer Circuit

An interesting function for some wireline applications is to receive a differential signal and yet maintain that signal as single-ended. This configuration is not easy to achieve with an operational amplifier because the input impedance is not balanced if an equalization circuit is used. [Figure 6](#) shows such a single-ended equalization circuit with an operation amplifier.

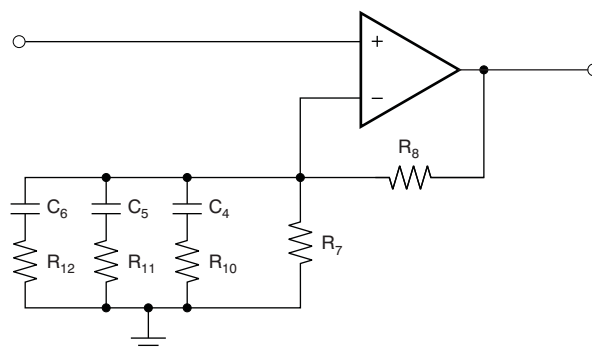


Figure 6. Single-Ended Equalizer Circuit

To achieve a differential input, single-ended output, equalization circuit requires two high-impedance inputs. The [VCA82x](#) family enables a very simple implementation of this function, as [Figure 7](#) illustrates.

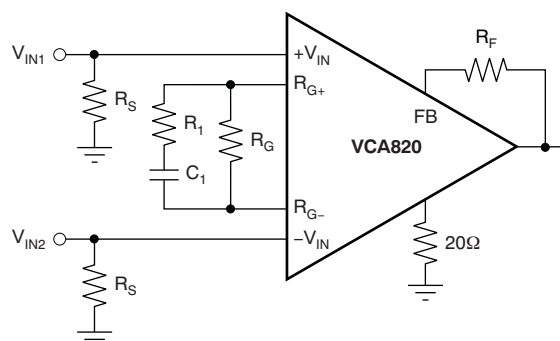


Figure 7. Differential Equalizer Circuit (VCA820)

A full cable equalizer for 100ft of a Belden 1694F coax cable is shown in [Figure 8](#).

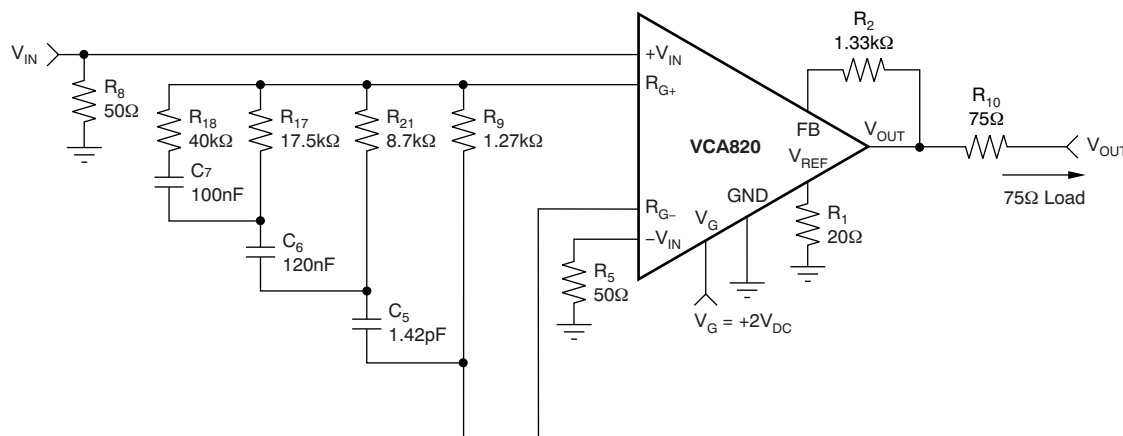


Figure 8. Equalizer Circuit for 100ft of Belden 1694F Coax Cable

This implementation has a maximum gain error of 0.2dB versus frequency from dc to 40MHz. We can then compare the frequency response of this circuit to the attenuation of the Belden 1694F coax cable; both responses are plotted together in [Figure 9](#).

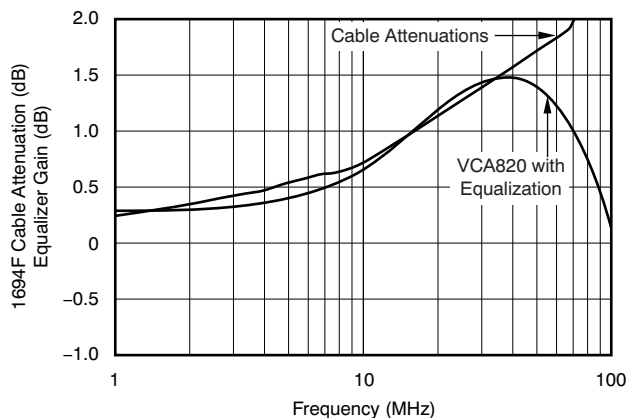


Figure 9. Cable Equalization and Cable Attenuation Comparison

3 Implementation Example

As an implementation example, we will use a Belden 8723 multi-conductor, shielded twisted-pair cable as a twisted pair, and evaluate its frequency response with a characteristic impedance of 52Ω. Note that because this twisted pair is recommended for both audio and control applications, we must evaluate its frequency response in order to determine the equalization. For this purpose, 100ft of cable was evaluated with the circuit shown in [Figure 10](#).

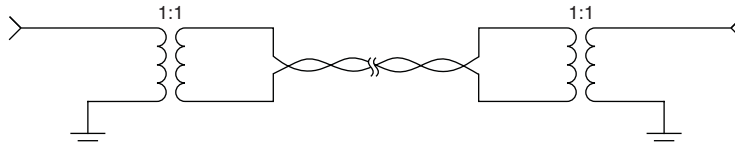


Figure 10. Twisted Pair Evaluation Circuit Model

The network analyzer is single-ended. Therefore, transformers are used at both the input and the output in order to realize the single-ended to differential conversion as well as the differential to single-ended conversion. The transformers are calibrated out to eliminate any influence on the measurement, as [Figure 11](#) shows.

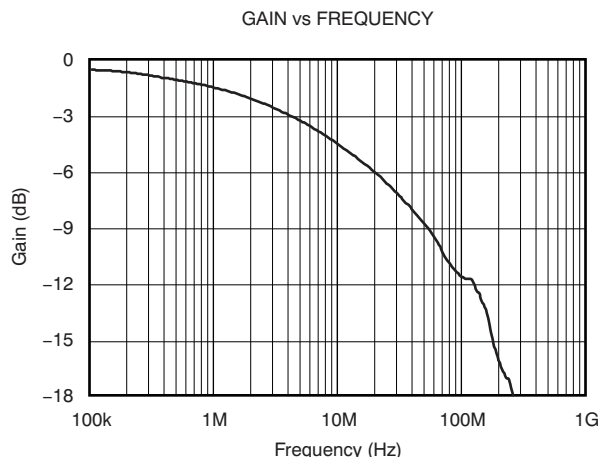


Figure 11. Belden 8723 Shielded Twisted-Pair Frequency Response

There are two notable points with this characteristic performance:

1. The insertion loss is 0.5dB.
2. The -3dB bandwidth is 4MHz.

To proceed with the design of both the transmission (Tx) and the reception (Rx) paths, first consider the signal we want to compensate for. The signal is differential on both the input and output, and is gained by 2V/V in the Tx path to compensate for back-matching losses. To simplify the design of the receiver, we use a differential noninverting configuration that requires a dual operational amplifier. This approach allows better Tx line matching over frequency because the amplifier input is high impedance and provides more variety in component selection. The proposed schematic is shown in Figure 12.

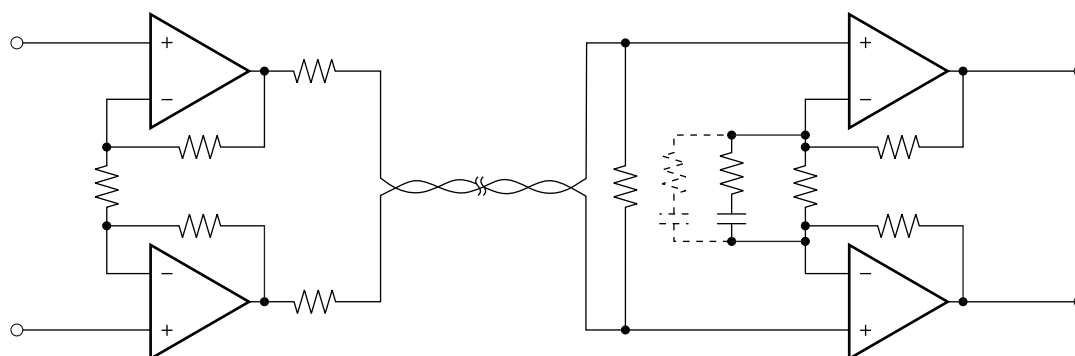


Figure 12. Proposed Tx and Rx Schematic

Notice that the gain curve can also be expressed as an attenuation and curve fitting a third-order gain function, to yield Figure 13, with poles located at 1.54MHz, 12.87MHz, and 141.1MHz.

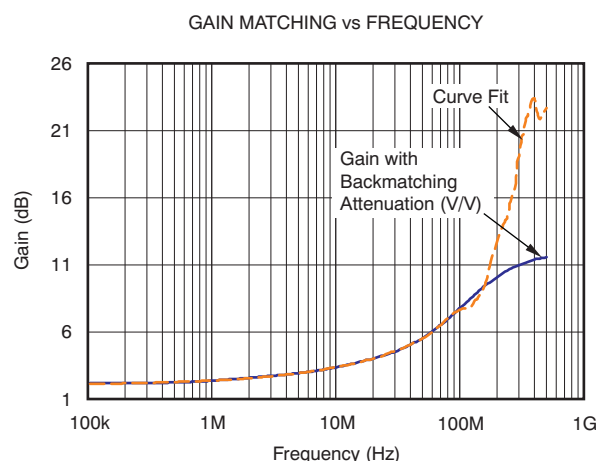


Figure 13. Theoretical Gain Matching to the Attenuation

The methodology used to determine the location of the poles is described in detail in the related application note, *A Numerical Solution to an Analog Problem* (SBOA124), available for download at www.ti.com.

In theory, if the amplifier has infinite bandwidth, the gain matches to 100MHz. In practice, however, as a result of the selected amplifier limitations and a conscious choice of over-compensating the amplifier for maximum flatness, the frequency compensation is limited to approximately 40MHz. The complete schematic for the developed Tx/Rx circuit, using an [OPA683](#) for both the Tx and the Rx functions, is given in [Figure 14](#); the corresponding performance measurement is shown in [Figure 15](#).

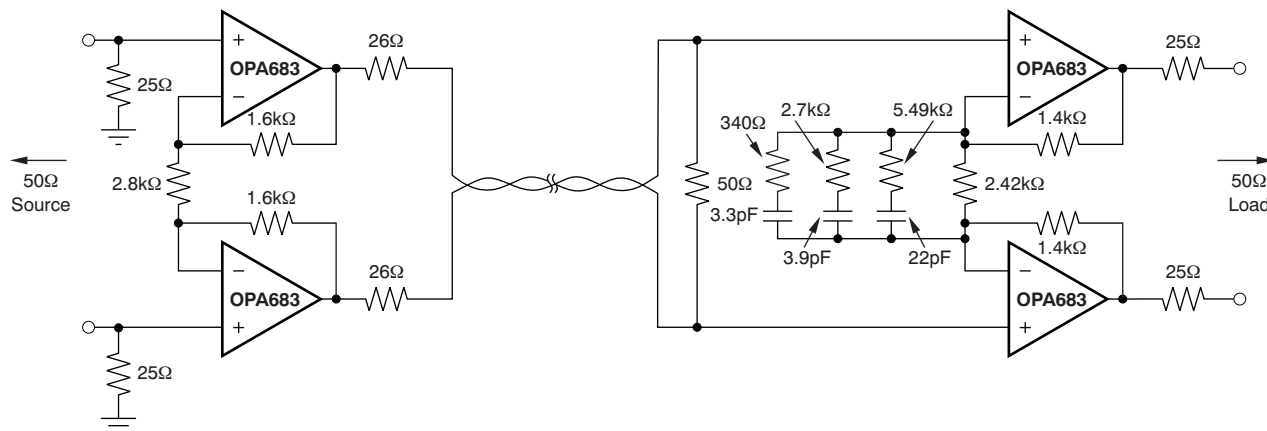


Figure 14. Developed Tx and Rx Circuit with the OPA683

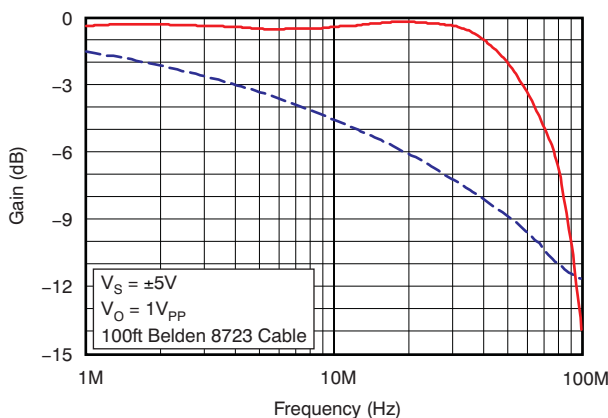


Figure 15. Measured Circuit Performance

The frequency response 0.2dB flatness is increased to greater than 30MHz and the -3dB increased from 4MHz to 55MHz.

4 Conclusion

This report provides some insights on the possible selections for either the transmission or the reception signal chain for typical wireline communications. It focuses on the application of equalization techniques and subsequent implementations with an example of performance improvement.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps